



In this example, a tilt switch is used (just like a button) as a digital input, and an LED is a digital output. The resistor is a pull-down resistor.
Related example:
<http://www.arduino.cc/en/Tutorial/TiltSensor>

