
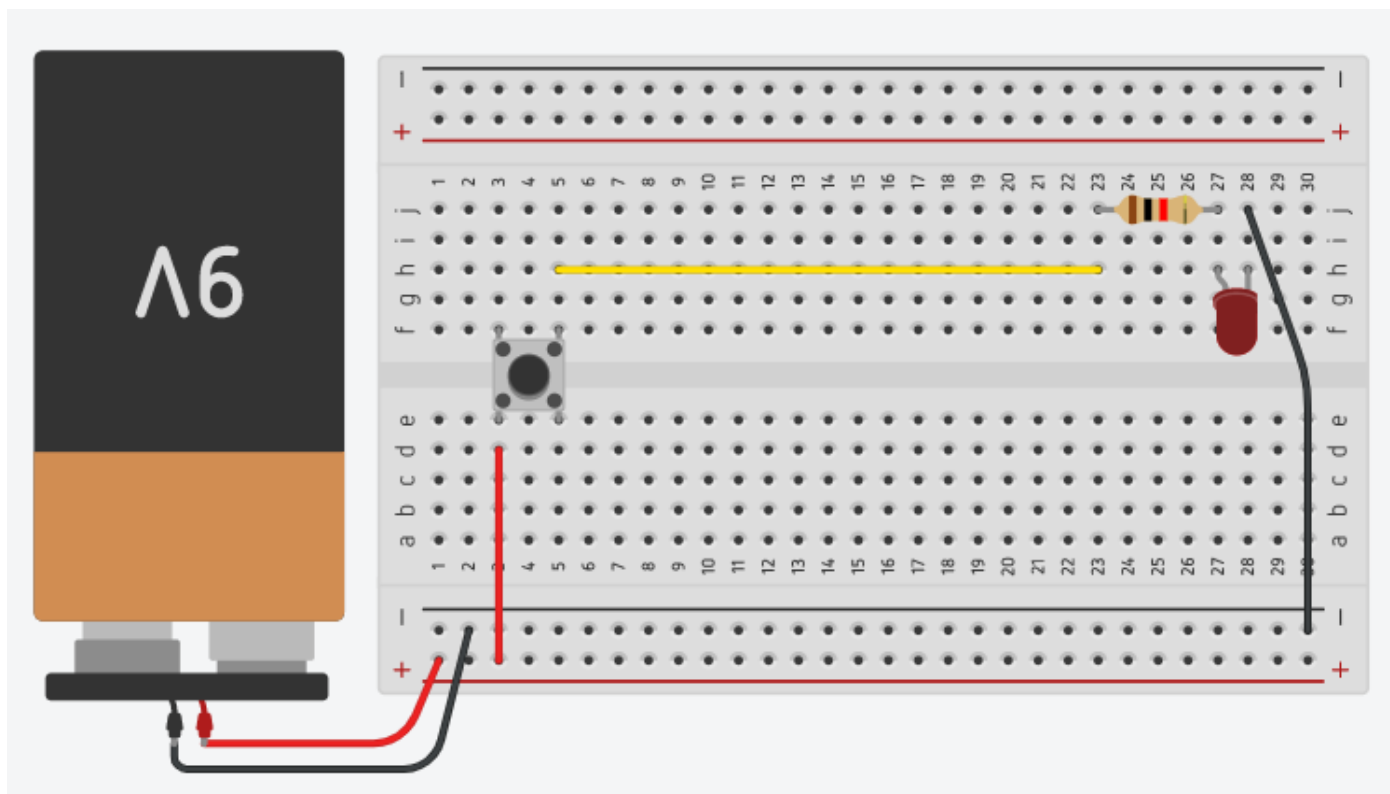


Esercitazioni di sistemi classe III AME

PORTE LOGICHE CON DIODI E TRANSISTOR

- 1- Simulare i circuiti assegnati con "ideal circuits" e ricavare la tabella della verità
- 2- Simulare i circuiti assegnati con "thinkercad"
- 3- Realizzare i circuiti su breadboard (lavorare a coppie sul banco)
- 4- Scrivere una relazione tecnica su quanto fatto.



IL PUSH BUTTON




 




Circuiti assegnati

livello basso = 0 = GROUND = TERRA



livello alto = 1 = Vcc = 5 volt

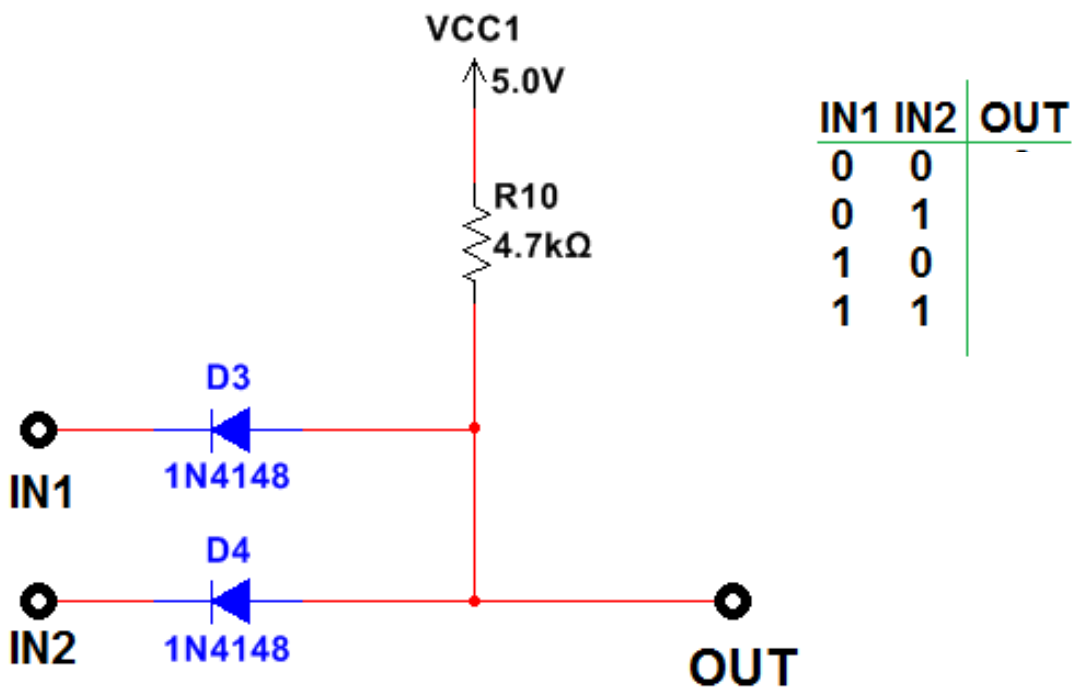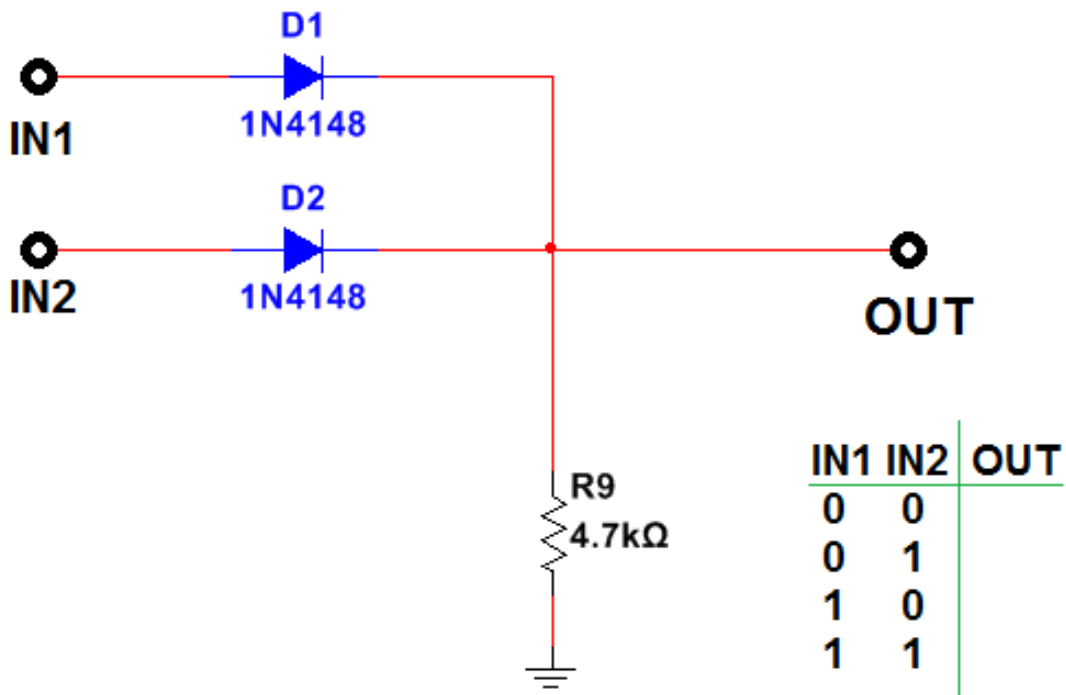

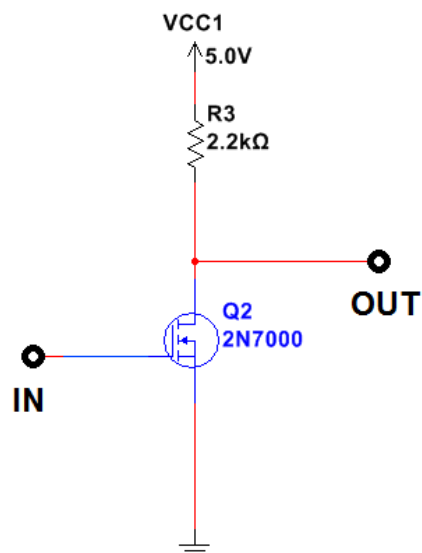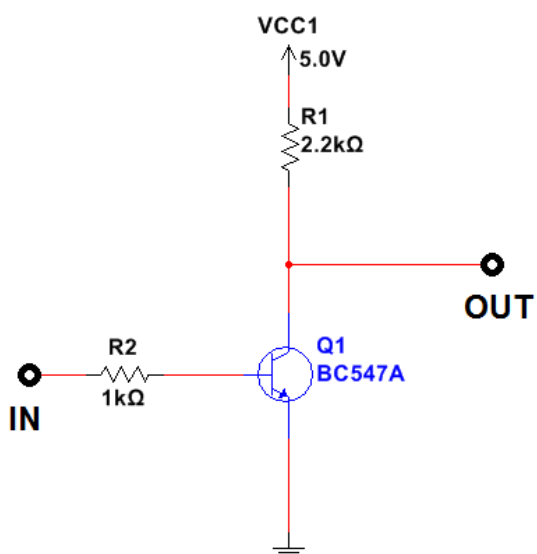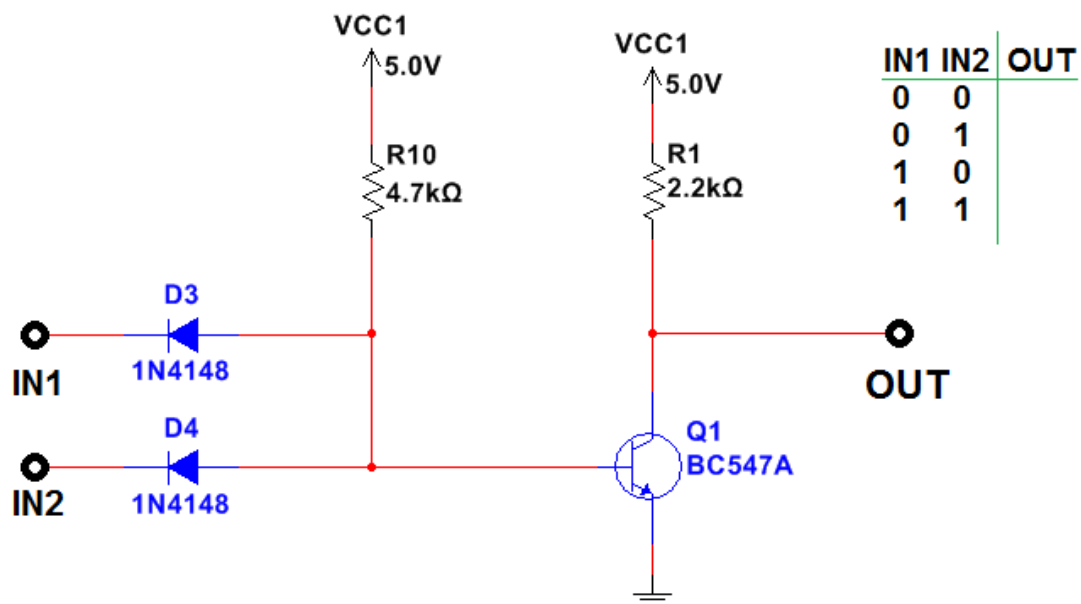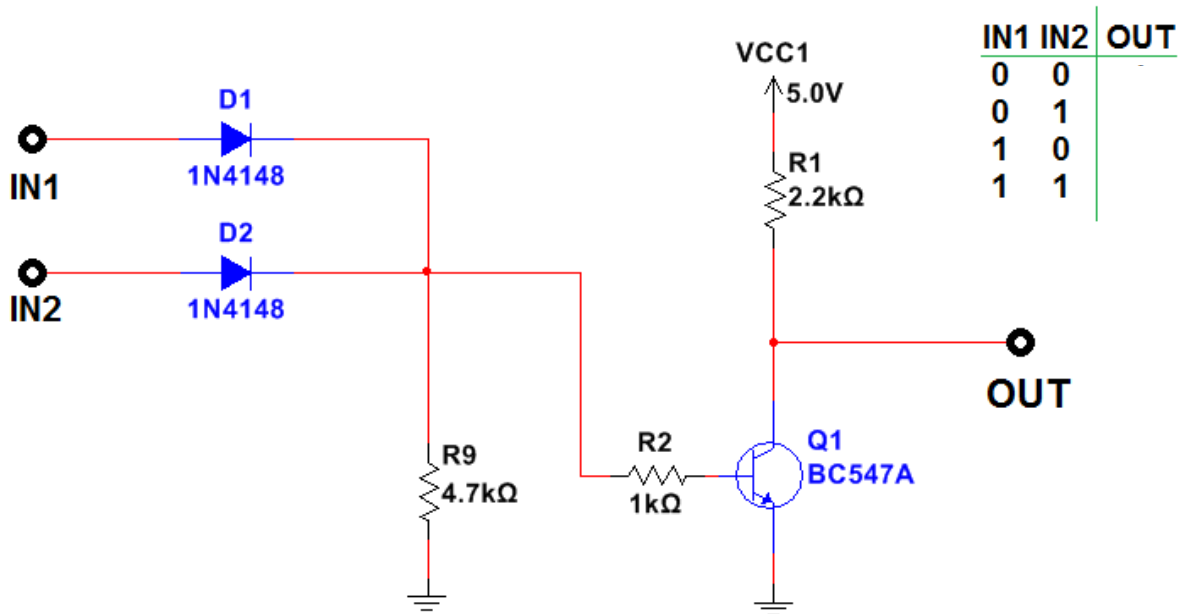

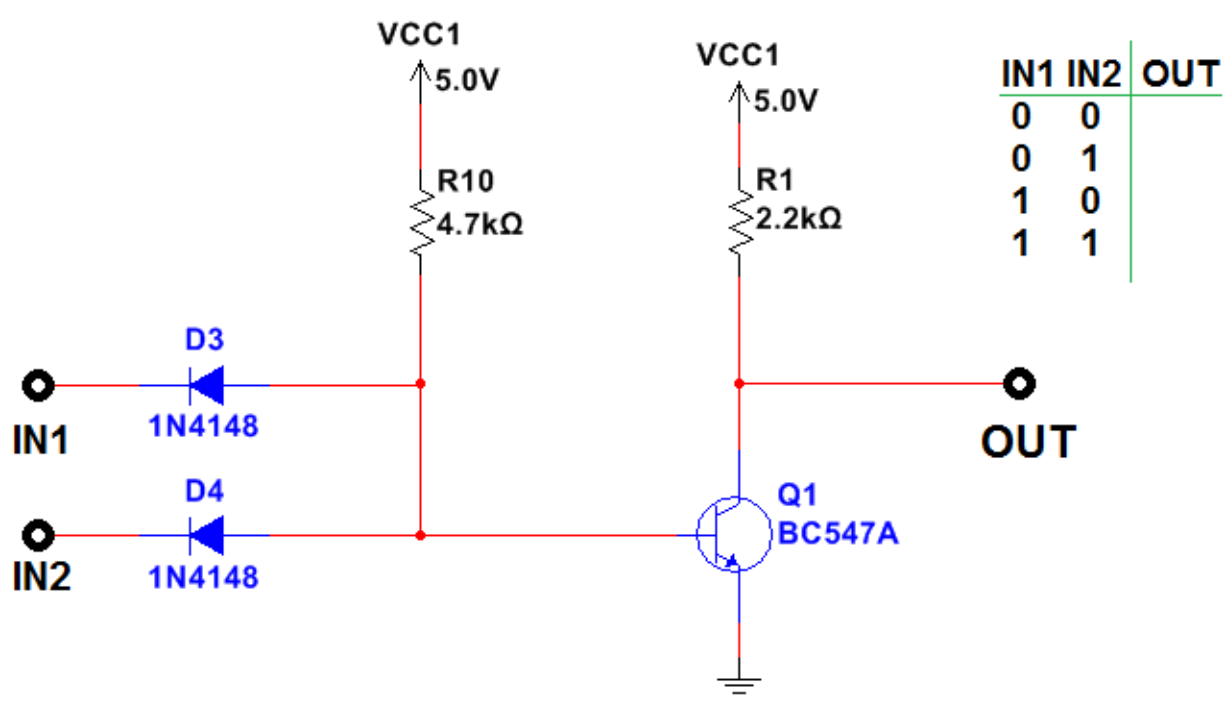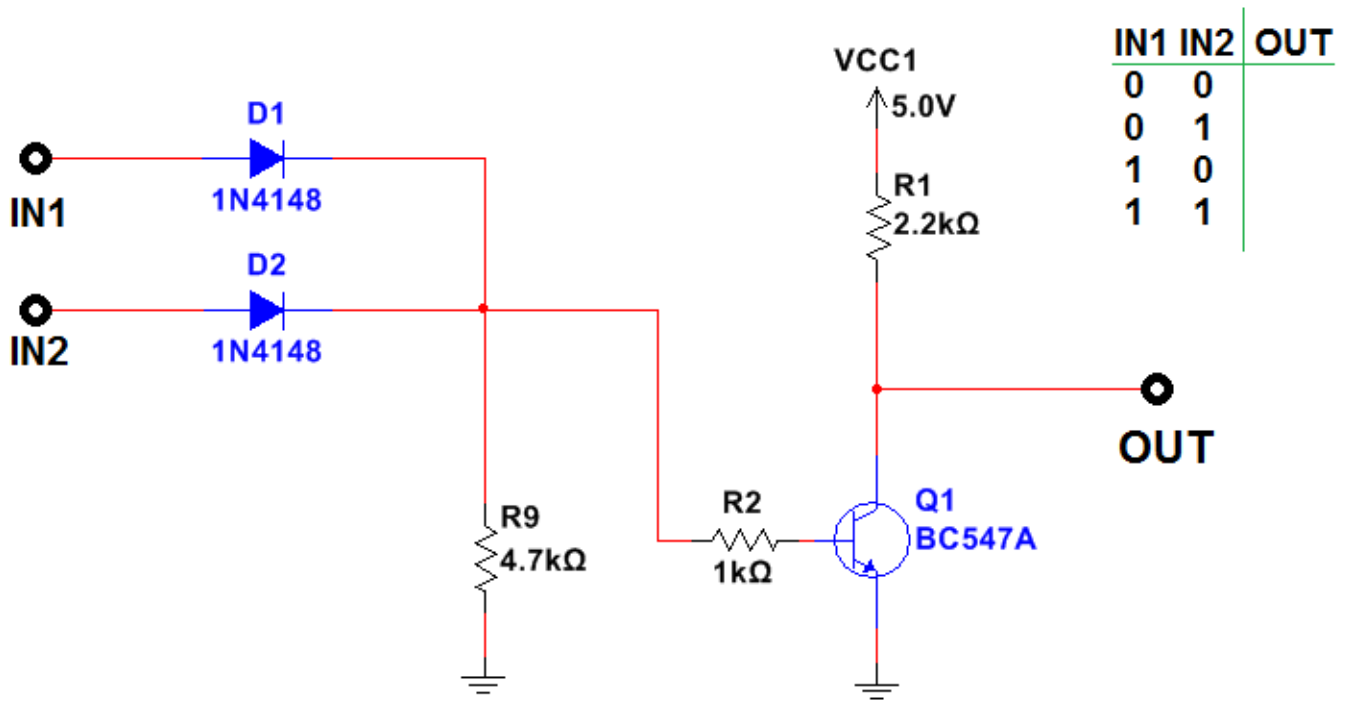

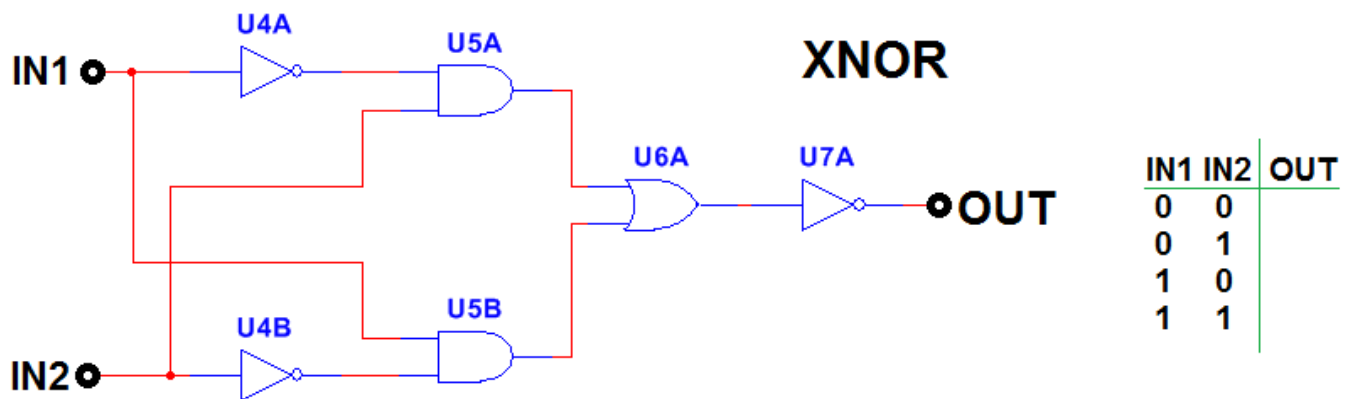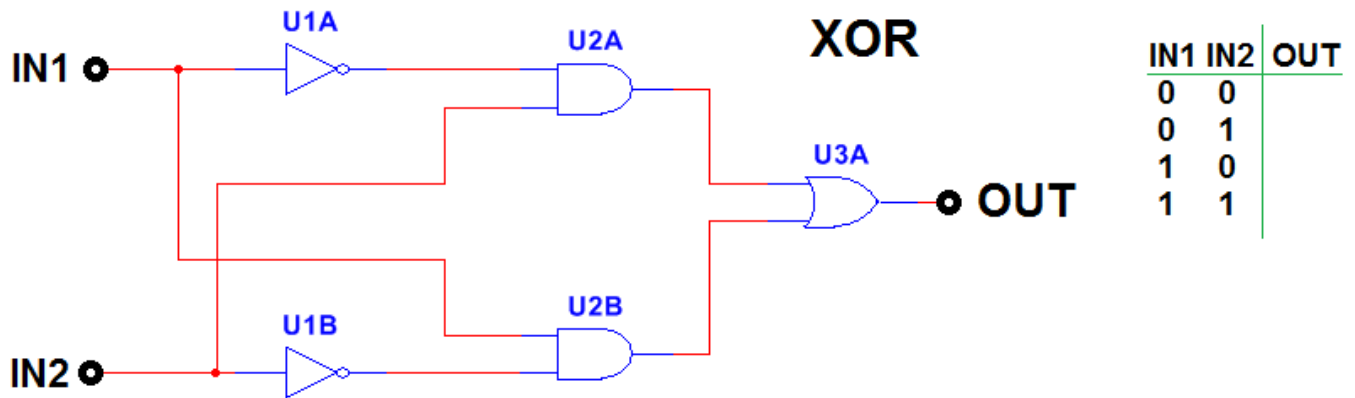Disegnare lo schema elettrico (con diodi e transistor) delle seguenti due porte e ricavare la tabella della verità




PORTE LOGICHE CON SOLI TRANSISTORS


- 1- Simulare i circuiti assegnati con “ideal circuits” e ricavare la tabella della verità
- 2- Simulare i circuiti assegnati con “thinkercad”
- 3- Realizzare i circuiti su breadboard (lavorare a coppie sul banco)
- 4- Scrivere una relazione tecnica su quanto fatto.

PORTA NOT

Step 1: NOT Gate


 


ù

 



PORTA AND

Step 3: AND Gate

 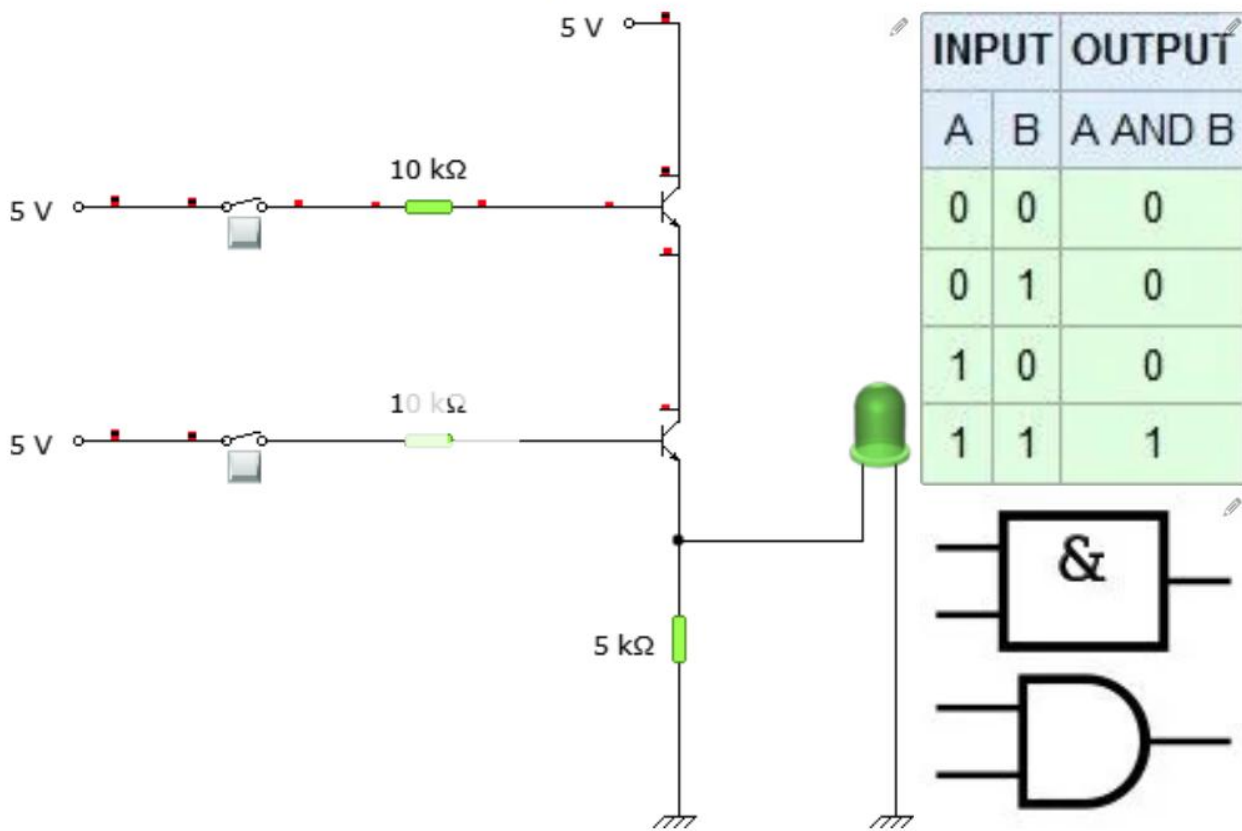



PORTA NAND

Step 5: NAND Gate

 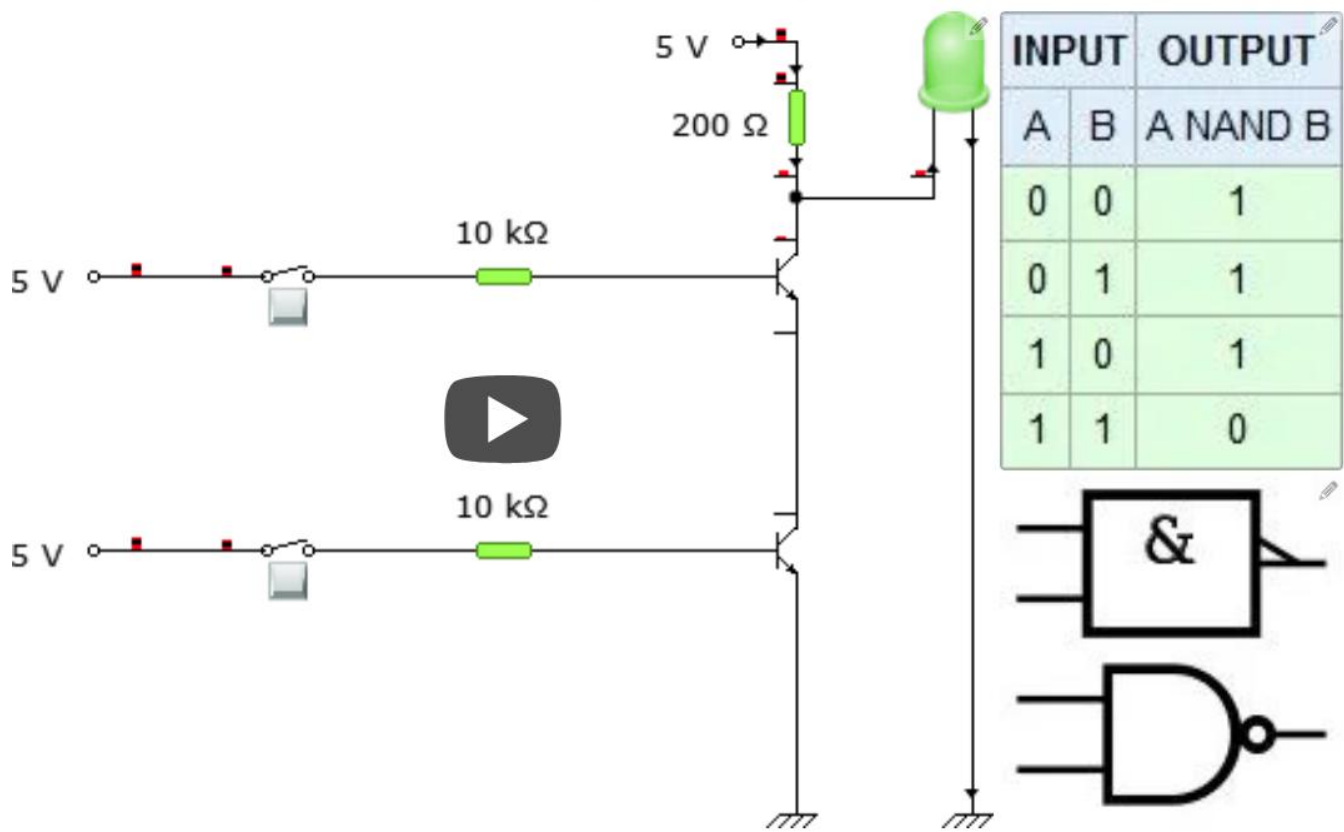



PORTA OR

Step 7: OR Gate

 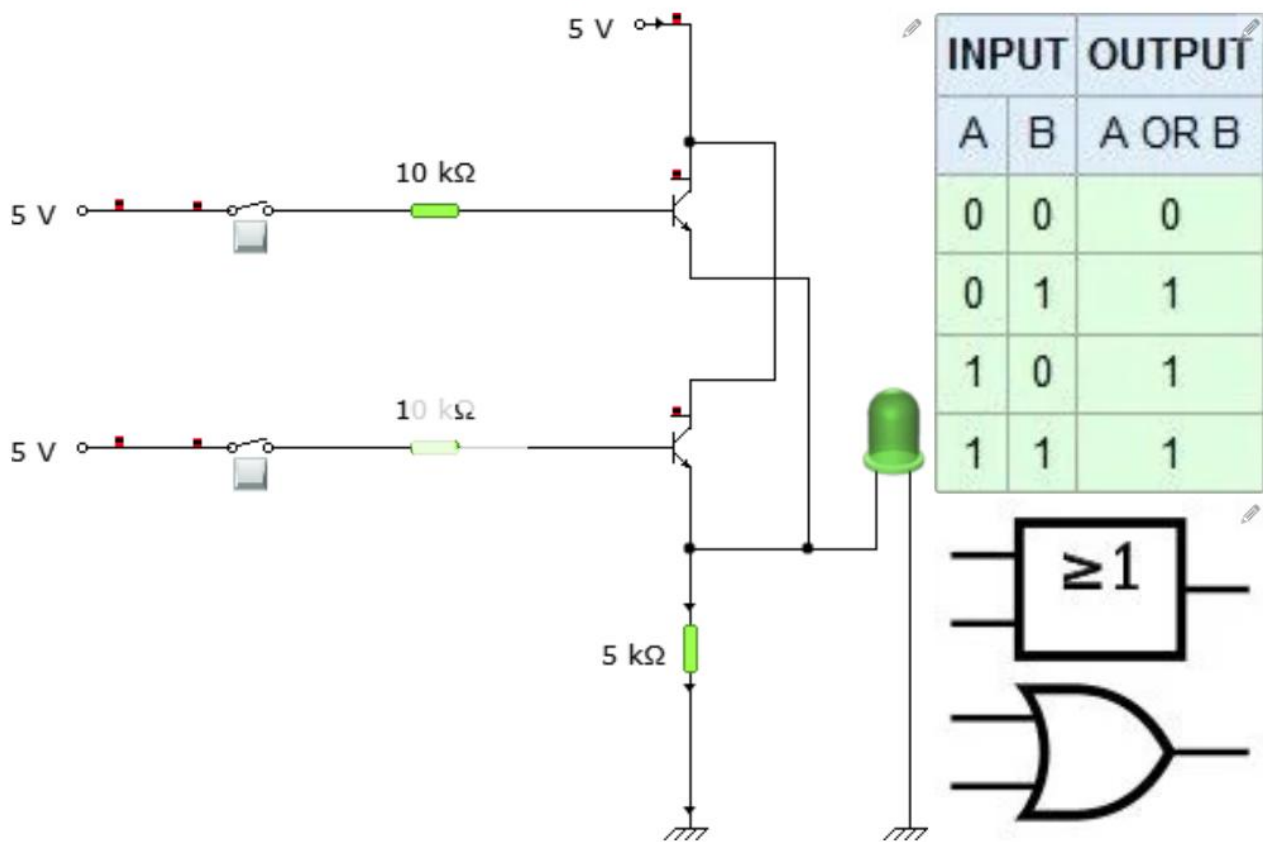


PORTA NOR

Step 9: NOR Gate

 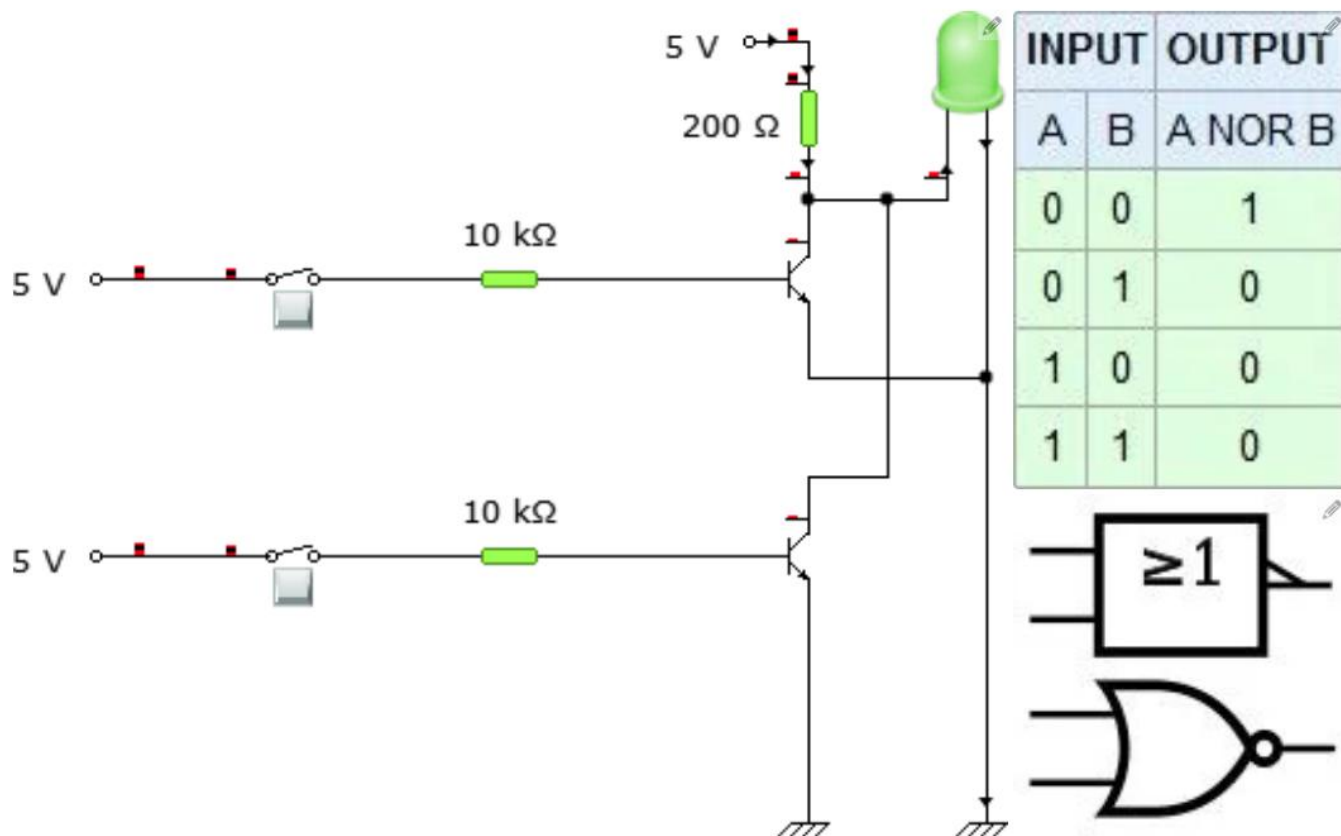


PORTA XOR e XNOR


Step 11: XOR Gate

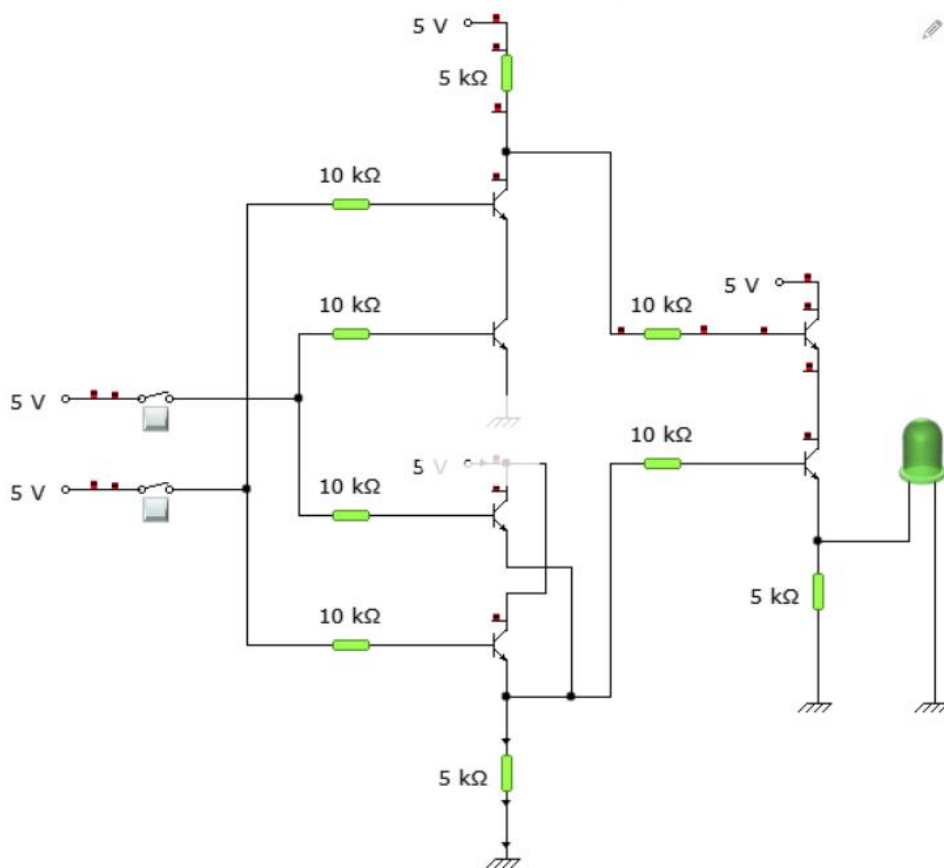


INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

 

Step 12: XNOR Gate

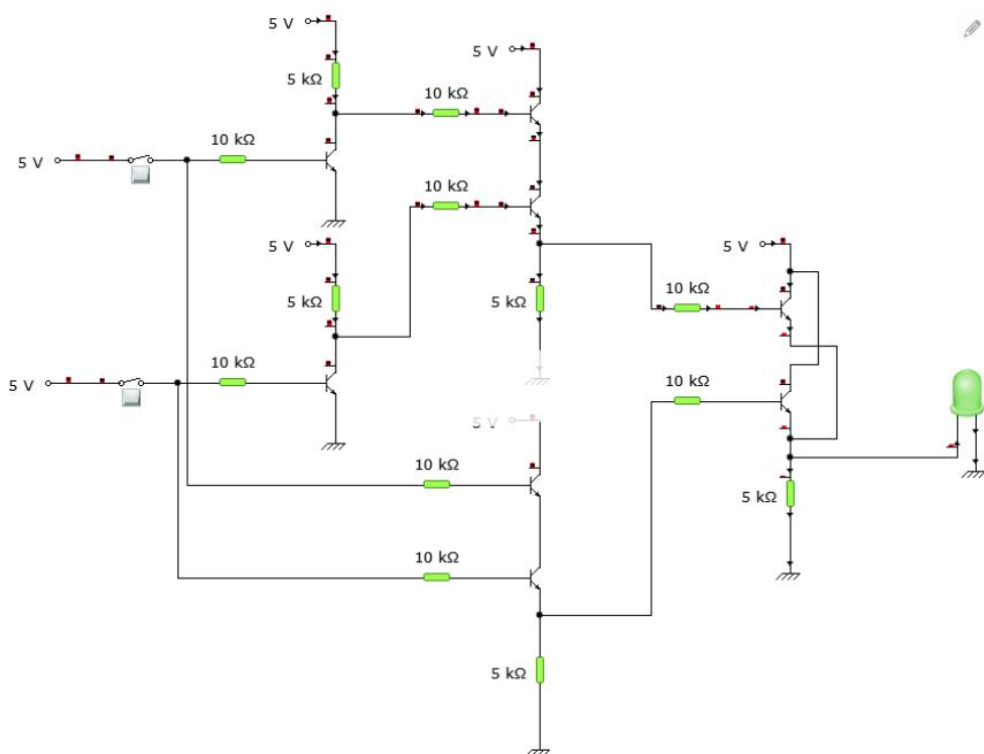


INPUT		OUTPUT
A	B	A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

 

Le memorie SR


Step 13: Build Something! - SR Flip-flop

 

(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

 

When using static gates as building blocks, the most fundamental latch is the simple SR latch, where S and R stand for set and reset. It can be constructed from a pair of cross-coupled NOR logic gates. The stored bit is present on the output marked Q.

The output usually marked as Q, but sometimes it is marked as X, Y or F.

While the S and R inputs are both low, feedback maintains the Q and Q' outputs in a constant state, with Q' the complement of Q. If S (Set) is pulsed high (=when you push the button) while R (Reset) is held low, then the Q output is forced high, and stays high when S returns to low; similarly, if R is pulsed high while S is held low, then the Q output is forced low, and stays low when R returns to low.