A simple touch switch can be created by using two NPN transistors. When touching the two blue cables, the LED will turn on.

AREF GND 3 2 1 0 9 8   7 6 5 4 3 2 1 0 TX RX
1 1 1 1   DIGITAL
PWM PWM PWM   PWM PWM PWM

L

TX
RX

Arduino   PWR

ICSP

PWR SEL   USB
EXT

www.arduino.cc

RESET   POWER   ANALOG IN
3V3 5V Gnd Vin   0 1 2 3 4 5

R2 1K   R3 10K

R1 10K

N   N

Made with [F] Fritzing.org